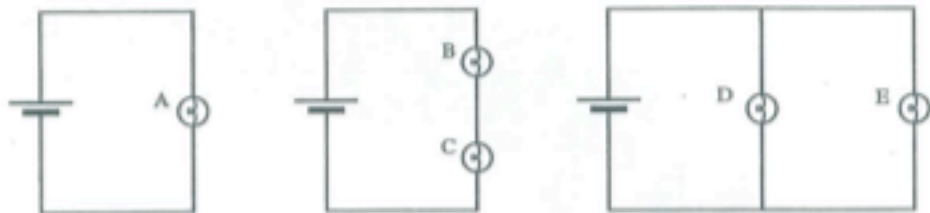


The circuits below contain identical bulbs and batteries. Rank the five bulbs in order of brightness from brightest to dimmest. If two or more bulbs are equal in brightness, indicate this in your response.

Explain the reasoning you used to determine this ranking.



Brightest

A

BC same

DE same

↳ also sharing energy source.

not sharing energy source.  
Sharing energy source  
so they are dividing the  
amount of energy necessary  
to light them.