

Physics 151

Prof. Thomson's Section

Solutions to Quiz on Ch 30

April 8, 2005


Consider the circuit below.

$$E = 10V$$

$$R_1 = 2\Omega$$

$$R_2 = 4\Omega$$

$$L = 6H$$

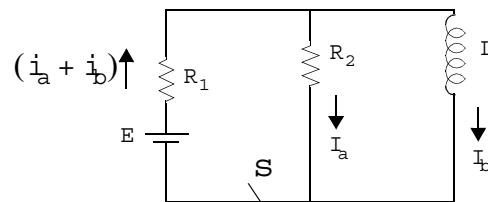

(a) Just after switch closed:

$$I_a = \frac{E}{(R_1 + R_2)} = \frac{10}{6} = 1.67A$$

 $I_a = 0A$ since inductor opposes changes in current and current can't change from 0 instantaneously.

$$(b) t = t_1 \quad i = 2.433A \quad \frac{di}{dt} = +0.570A/s$$

$$U = \frac{1}{2}Li^2 = \frac{1}{2} \times 6 \times (2.433)^2 = 17.8 \text{ joules}$$

(c) Long time after, inductor gives no resistance. - current flows thru inductor $\frac{Ldi}{dt} = 0$

$$i_a = 0$$

$$i_b = \frac{E}{R_1} = \underline{\underline{5A}}$$

(d) $I_a = I_b = \underline{\underline{5A}}$ just after \$S\$ re-opened.